
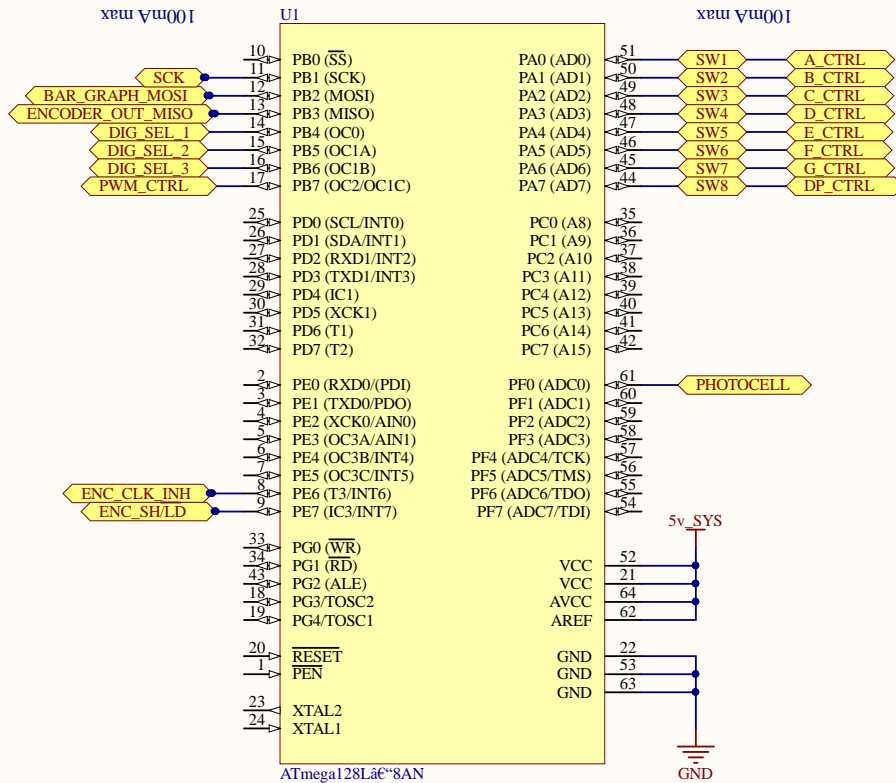



## Microcontroller

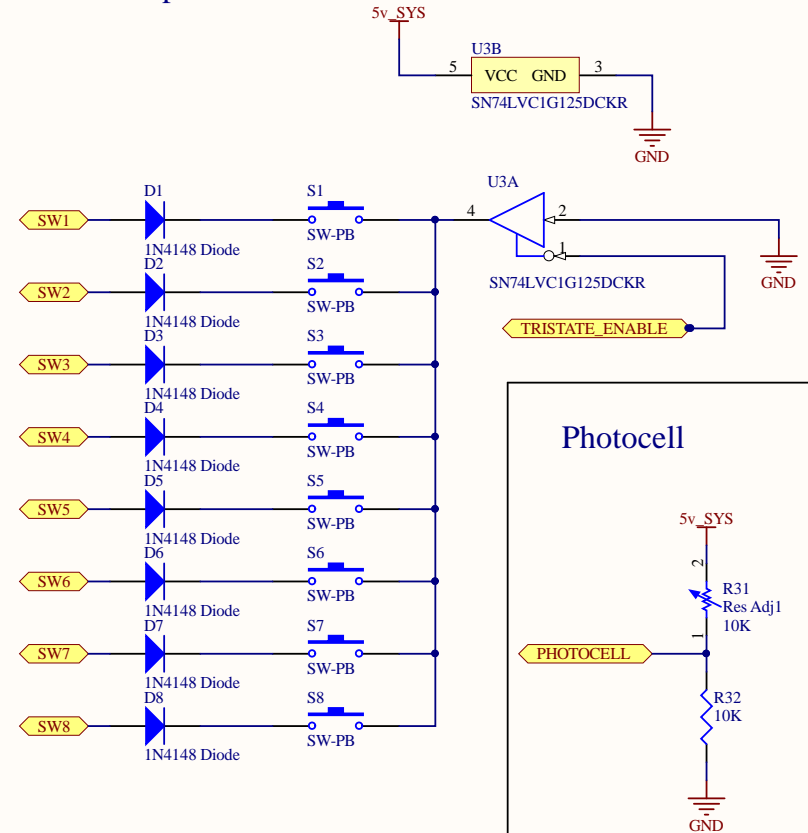


## Button Inputs



## Photocell

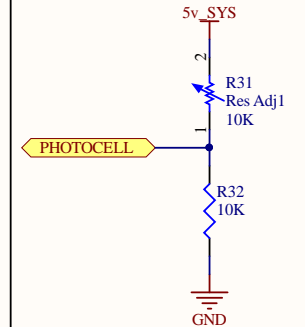


Microcontroller and Switches			Nick McComb <a href="http://www.nickmccomb.net">www.nickmccomb.net</a>
Size: A4	Number: 1	Revision:	
Date: 11/7/2016	Time: 9:22:12 PM	Sheet 1 of 4	
File: C:\Users\Nick\Documents\GitHub\ECE473\lab4\sch\lab2\uC.SchDoc			

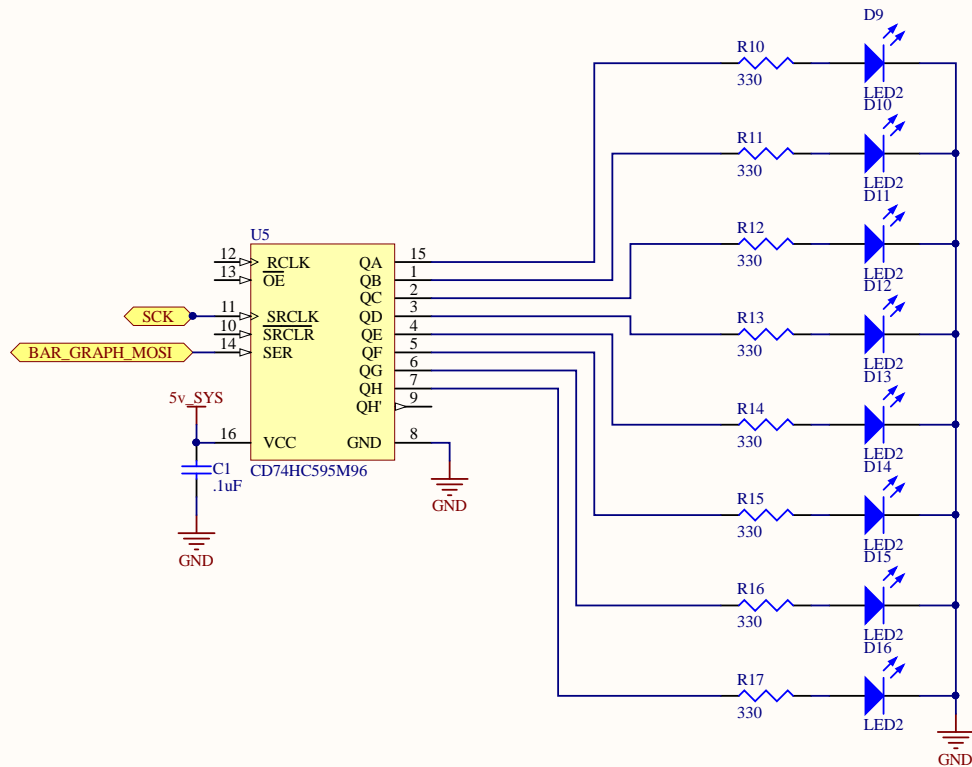

Title Bar Graph			www.nickmccomb.net	
Size: A4	Number:2	Revision:		
Date: 11/7/2016	Time: 9:22:12 PM	Sheet 2 of 4		
File: C:\Users\Nick\Documents\GitHub\ECE473\lab4\sch\lab2\barGraph.SchDoc				

## 7 Segment Control

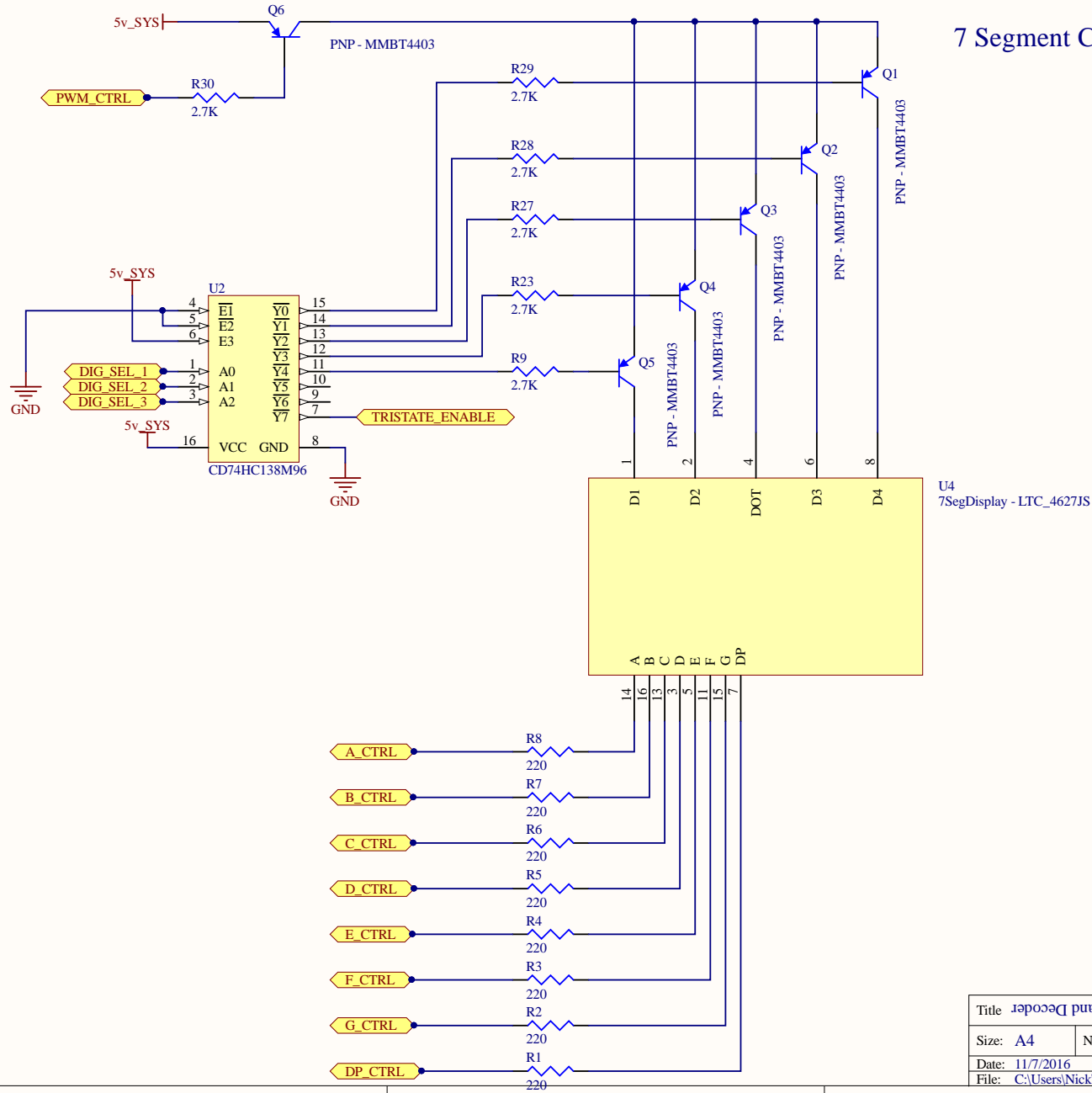

Title 7 Segment and Decoder			www.nickmccomb.net Nick McComb	
Size: A4	Number:3	Revision:		
Date: 11/7/2016	Time: 9:22:12 PM	Sheet 3 of 4		
File: C:\Users\Nick\Documents\GitHub\ECE473\lab4\sch\lab2\7Seg.SchDoc				

