

## Lab 2 Calculations and Measurements

### LED Current Limiting Resistor

The maximum current that we can move through Port A is 100mA, so the maximum that can move through a LED segment is 12.5mA (assuming they are all on at once, 100mA / 8 is 12.5mA).

That leads to the following calculations for resistor sizing:

$$5v - .2 * 2 \text{ (assumption for BJT } V_{CE}) - 2v \text{ (LED, from datasheet)} = 2.6$$

$$V = IR$$

$$\frac{2.6v}{.0125mA} = 208\Omega$$

From this, we can assume a real world value of 220Ω as a starting value.

**Current was measured at 11mA**, which is very close to our desired value. It is lower (which is definitely desired)

### PWM Biasing Resistor

To bias the BJTs, we need to select a value that can ensure the transistor is saturated during the entire operating range (from all the LEDs being turned off to them all being on). A 2mA current through the base will ensure this, according to the Datasheet. The following math considers the drops by the BJTs.

$$5v - .7v = 4.3v$$

$$\frac{4.3v}{2mA} = 2150\Omega$$

For the other biasing transistors (for the digit select), the math is very similar:

$$5v - .1v - .7v = 4.2v$$

$$\frac{4.2v}{2mA} = 2100\Omega$$

These values were rounded up to 3.3K due to resistor availability, but this value was checked to work as well.

### Measured Duty Cycle

Total period:  $3.03mS$

Total Duty Cycle:  $\frac{750\mu S}{3.03mS} = 24.75\%$